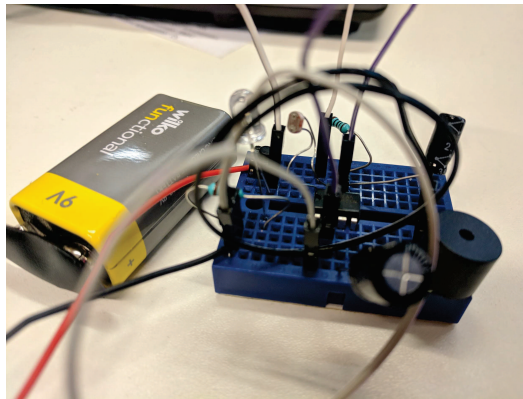


# Breadboard Musical Instrument


A workshop for



By Joe Brown

13th Feb 2019


Parts needed:

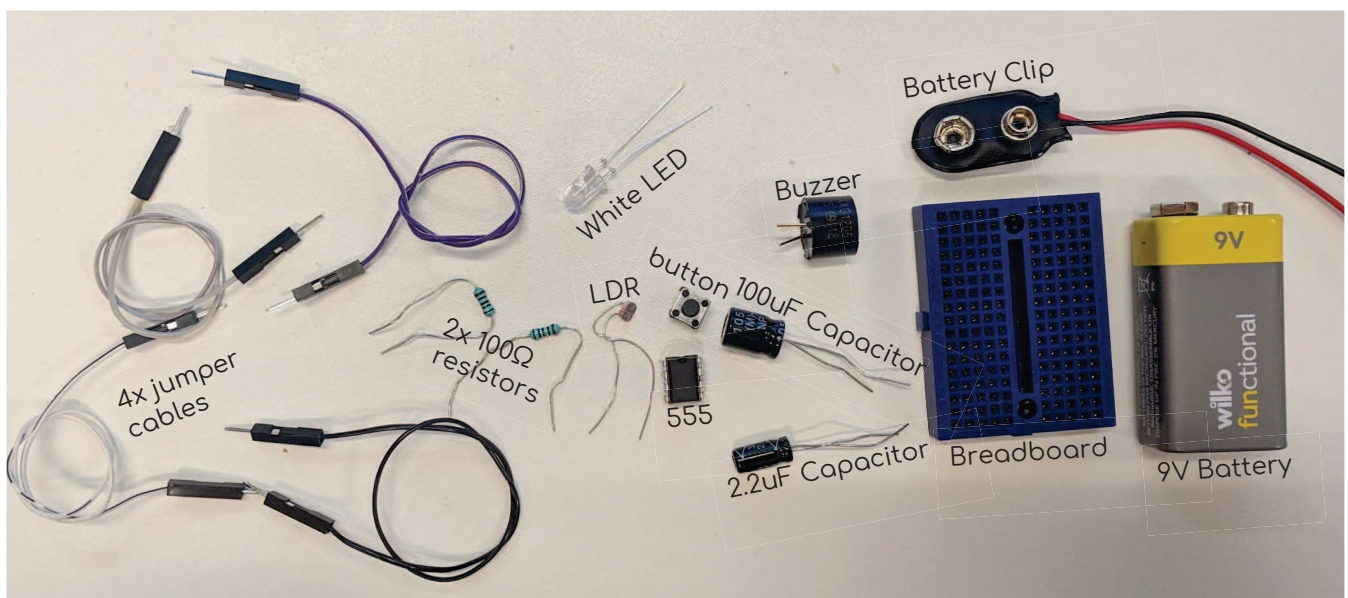

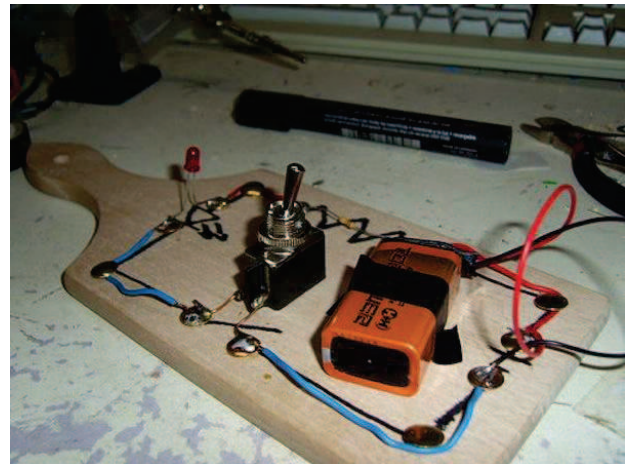
# Why BreadBoard?

Early electronic circuits were made using nails and wires connected to spare breadboards normally used for slicing bread!

The nickname stuck as new more suitable boards for electronics were made.




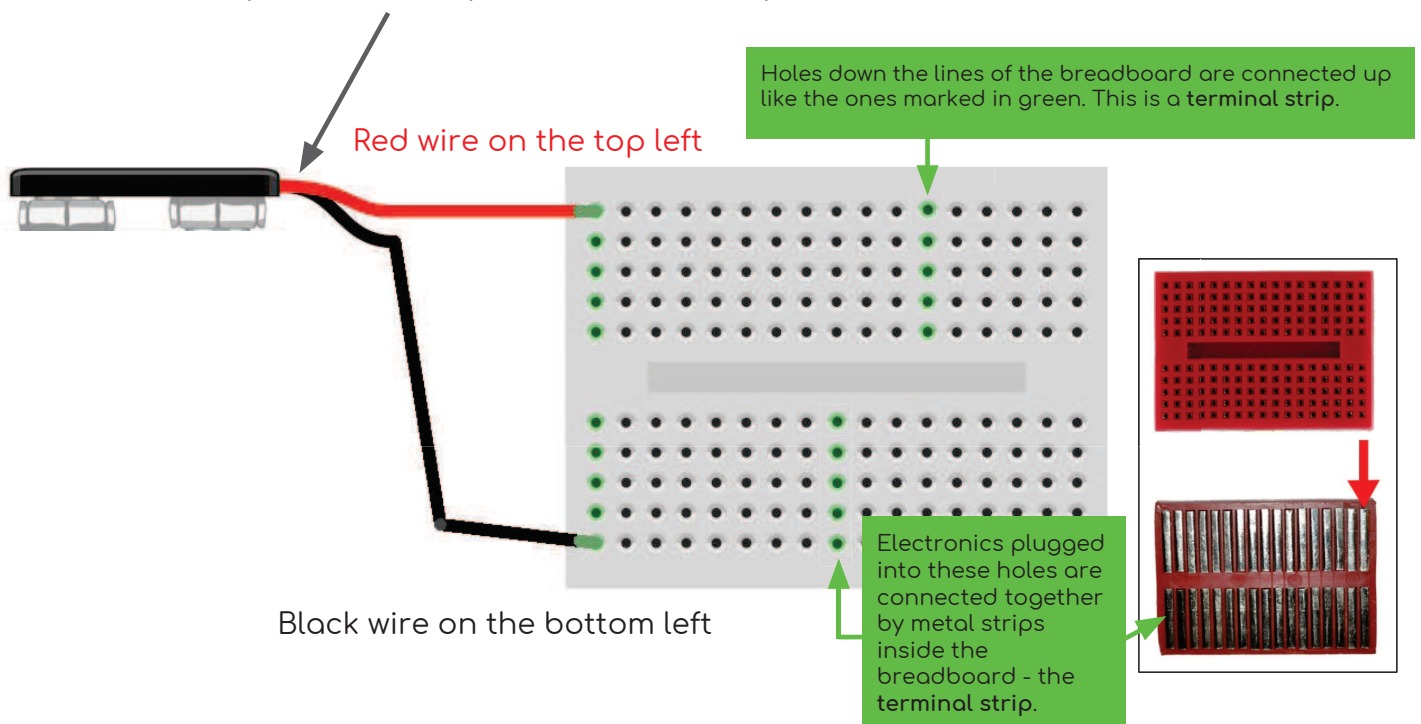1: Connect your battery connector to your breadboard.



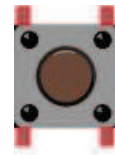2: Add the button.

Line it up vertically  
With the red battery wire




Position your  
button  
this way round

The button on the switch  
will be used to 'play' or  
'strum' your instrument!

3: Add 555 in middle of the breadboard, with the notch on the left

Notch on  
One side

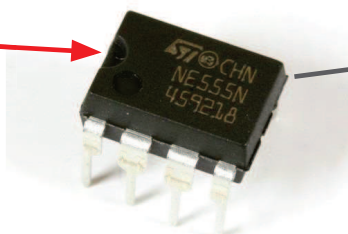


A 555 is a chip that produces  
pulses and in the case of our  
musical instrument it will be  
generating the sounds!




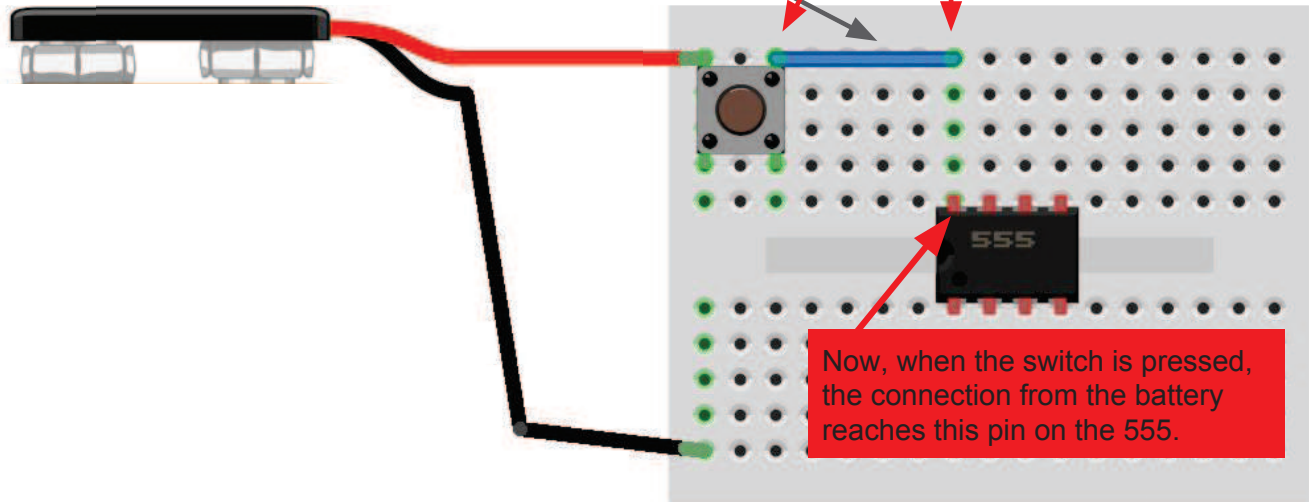
4: Add wire connecting the switch to the 555

Any colour of wire will work!  
Push each end of the wire into holes in the breadboard




5: Add the LED connected to the switch.

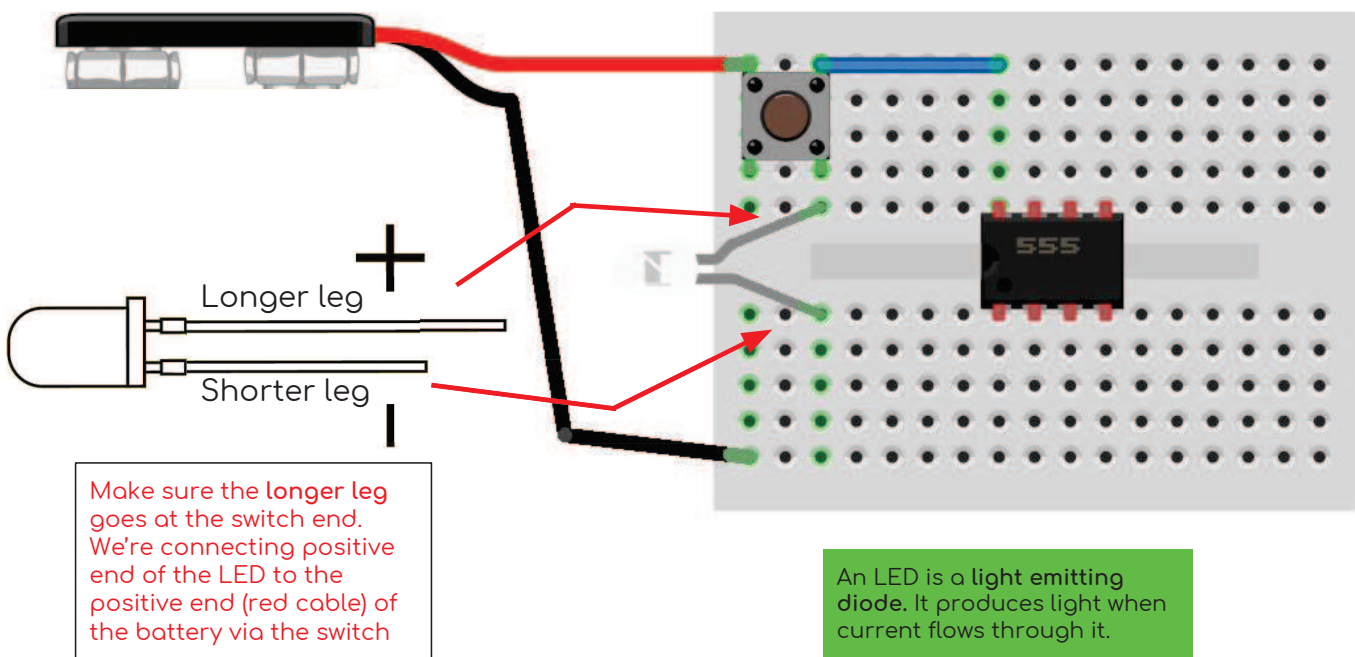

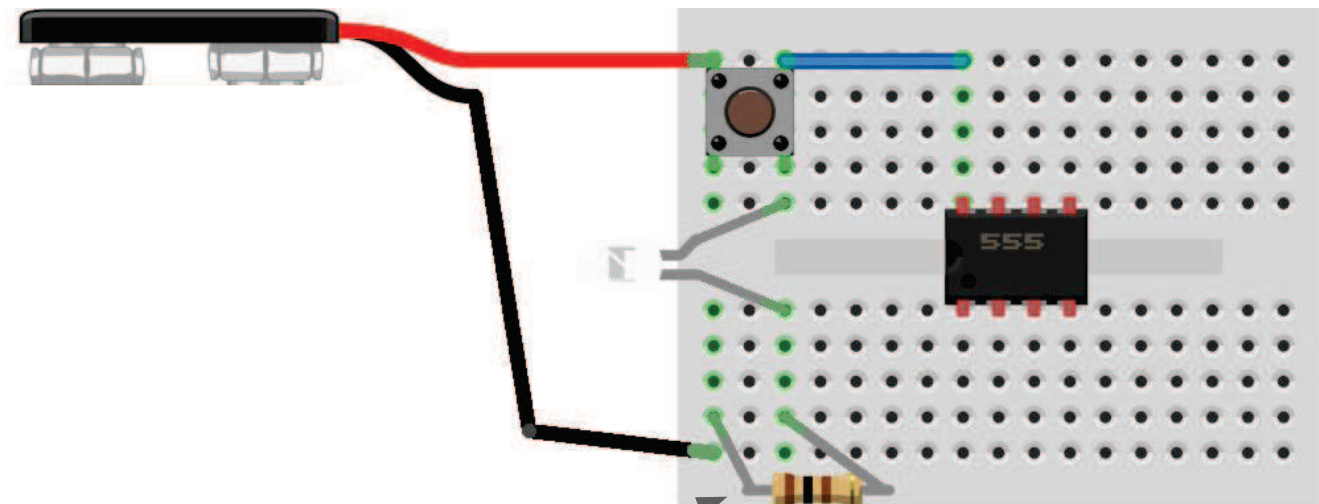

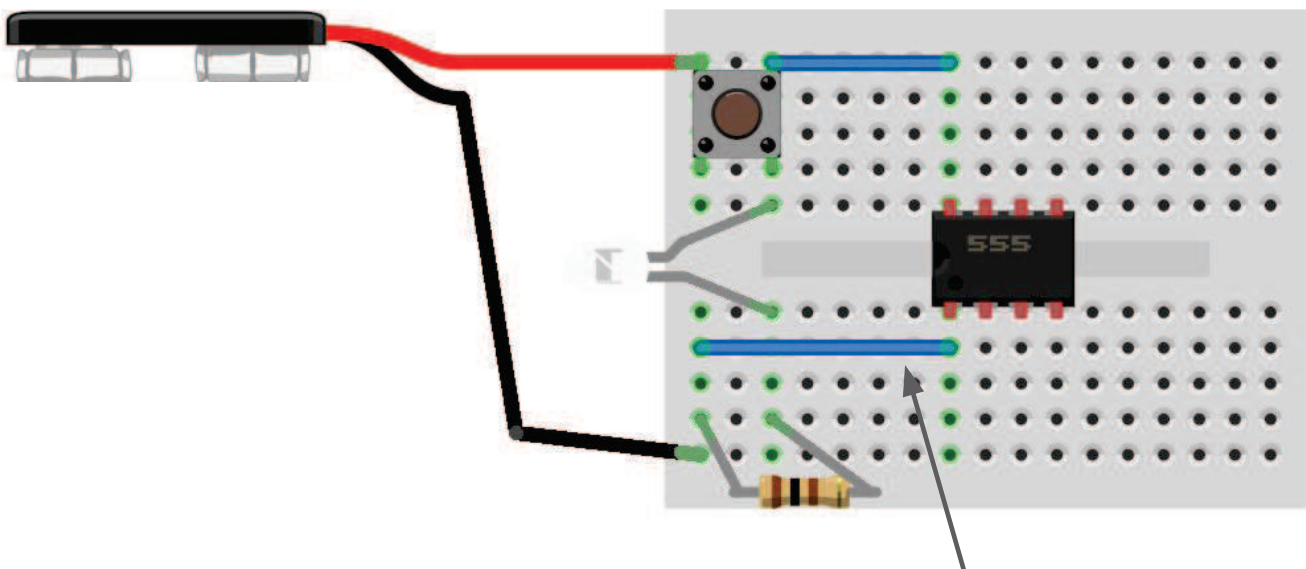
6: Add a resistor connecting the LED to the black (negative) battery cable

Remember components are connected together vertically along the terminal strip. See the green holes.






7: Add a wire connecting the black (negative) battery cable to the 555

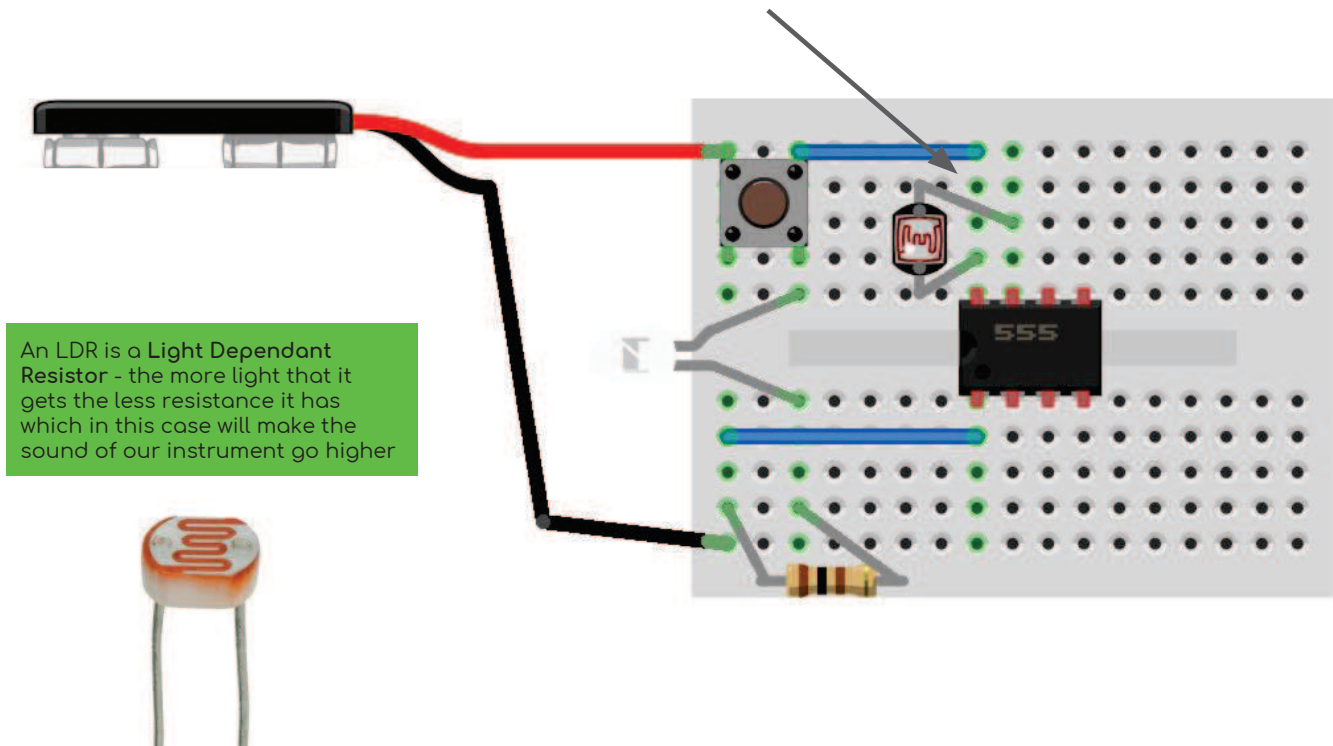8: Connect the LDR to the switch and the 555




9: Add a resistor by the 555

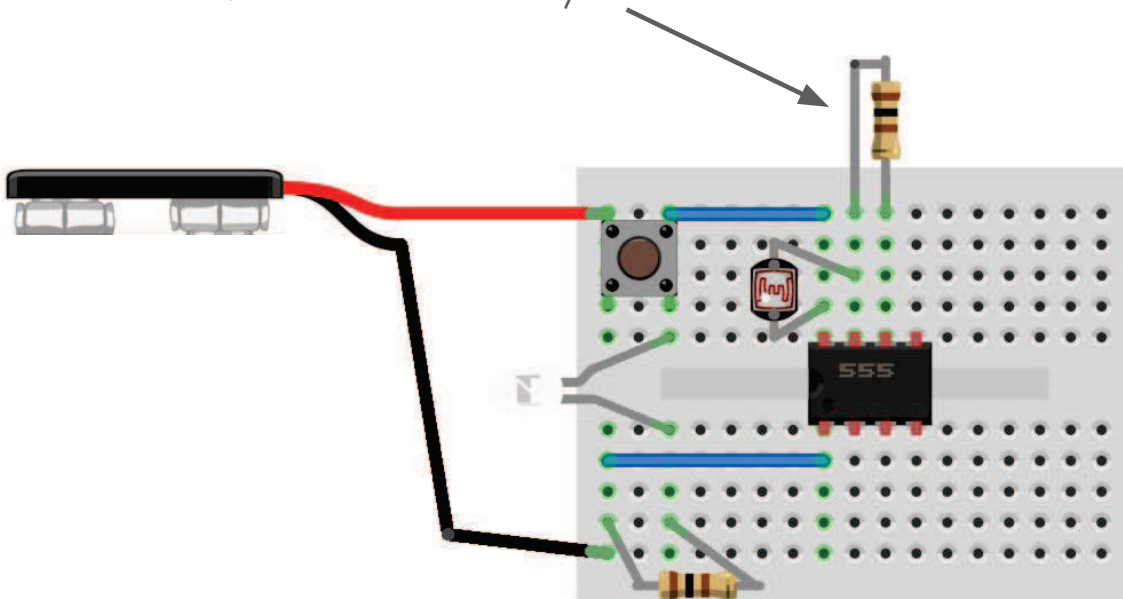


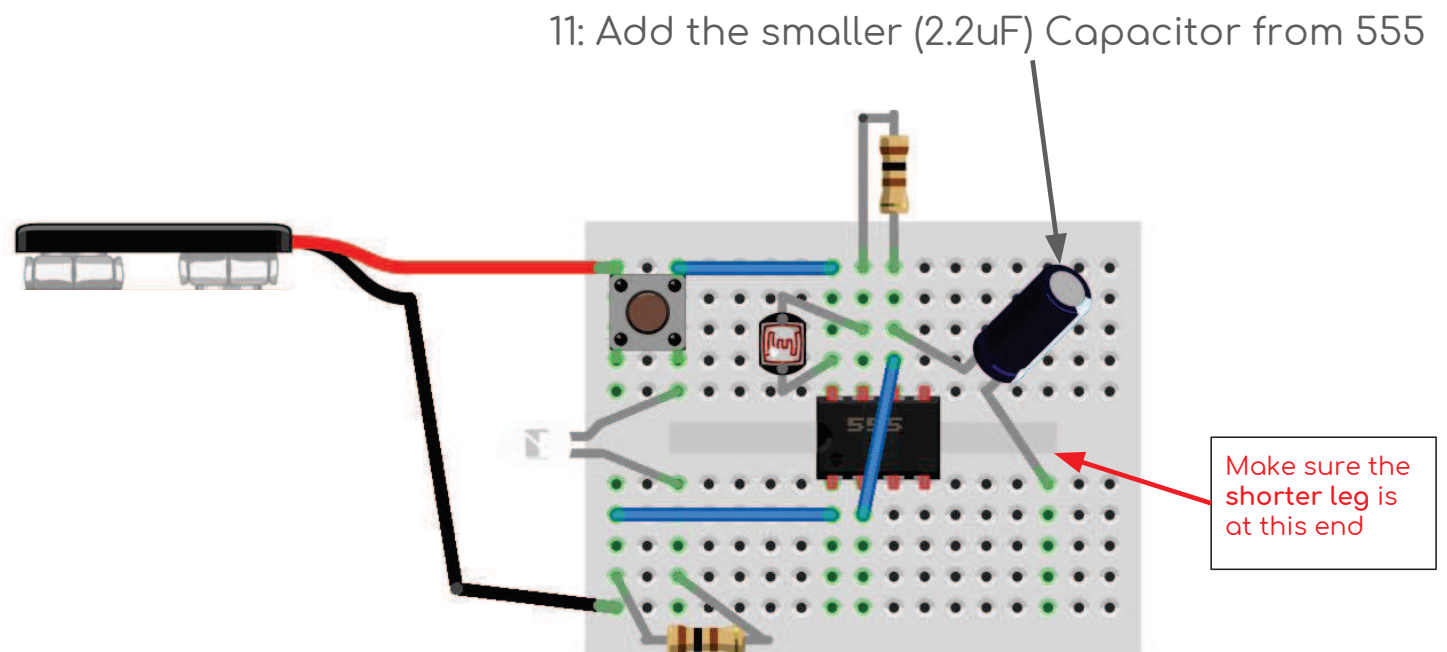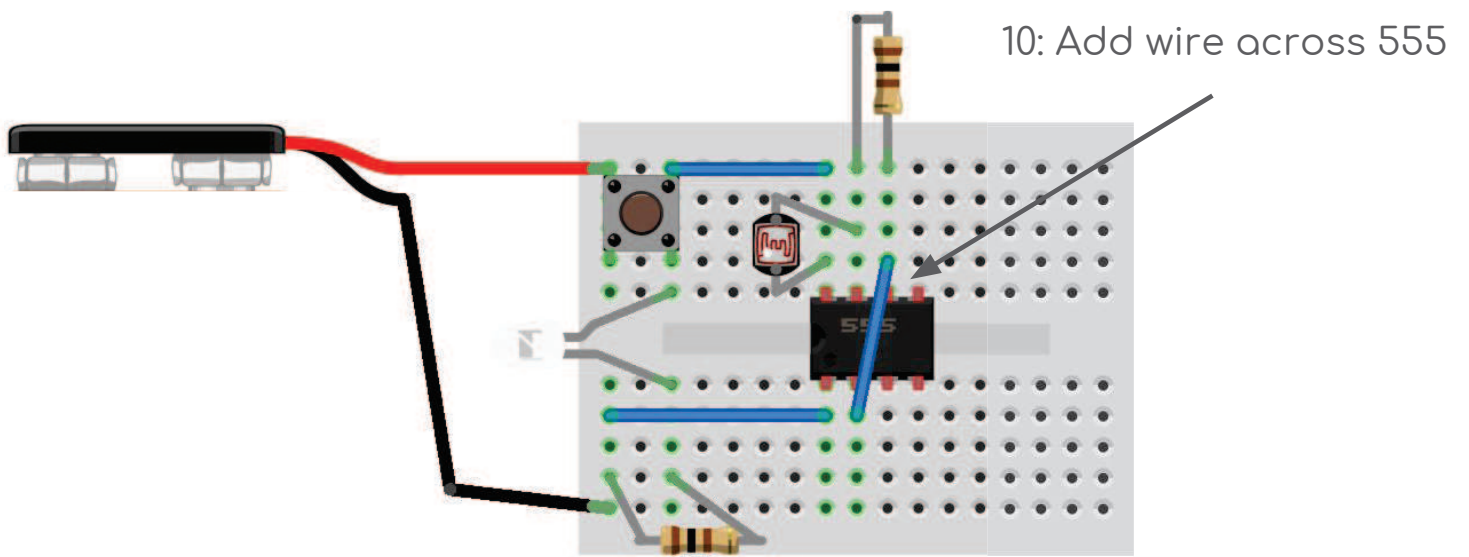



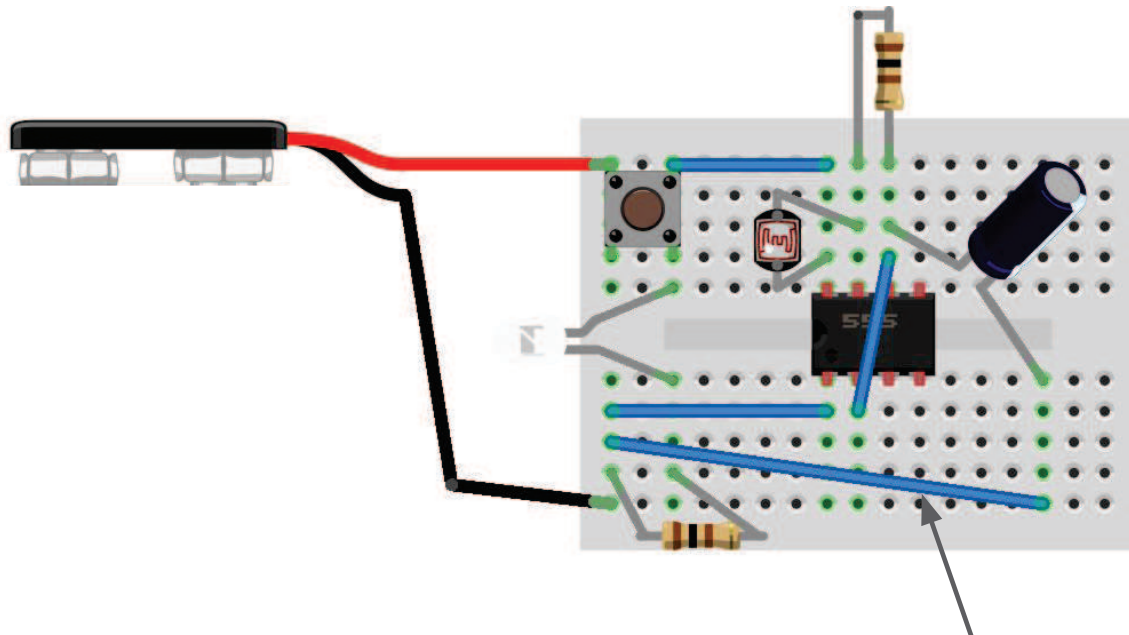

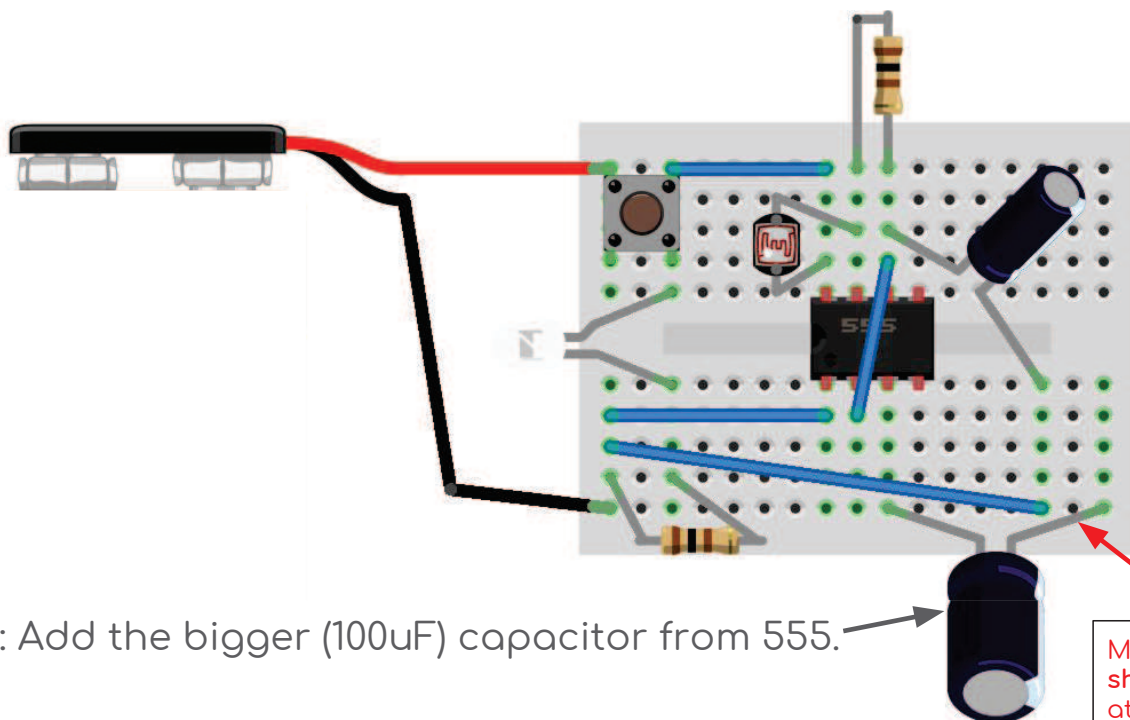12: Add wire from the black (negative) battery to the capacitor




13: Add the bigger (100uF) capacitor from 555.


Make sure the shorter leg is at this end




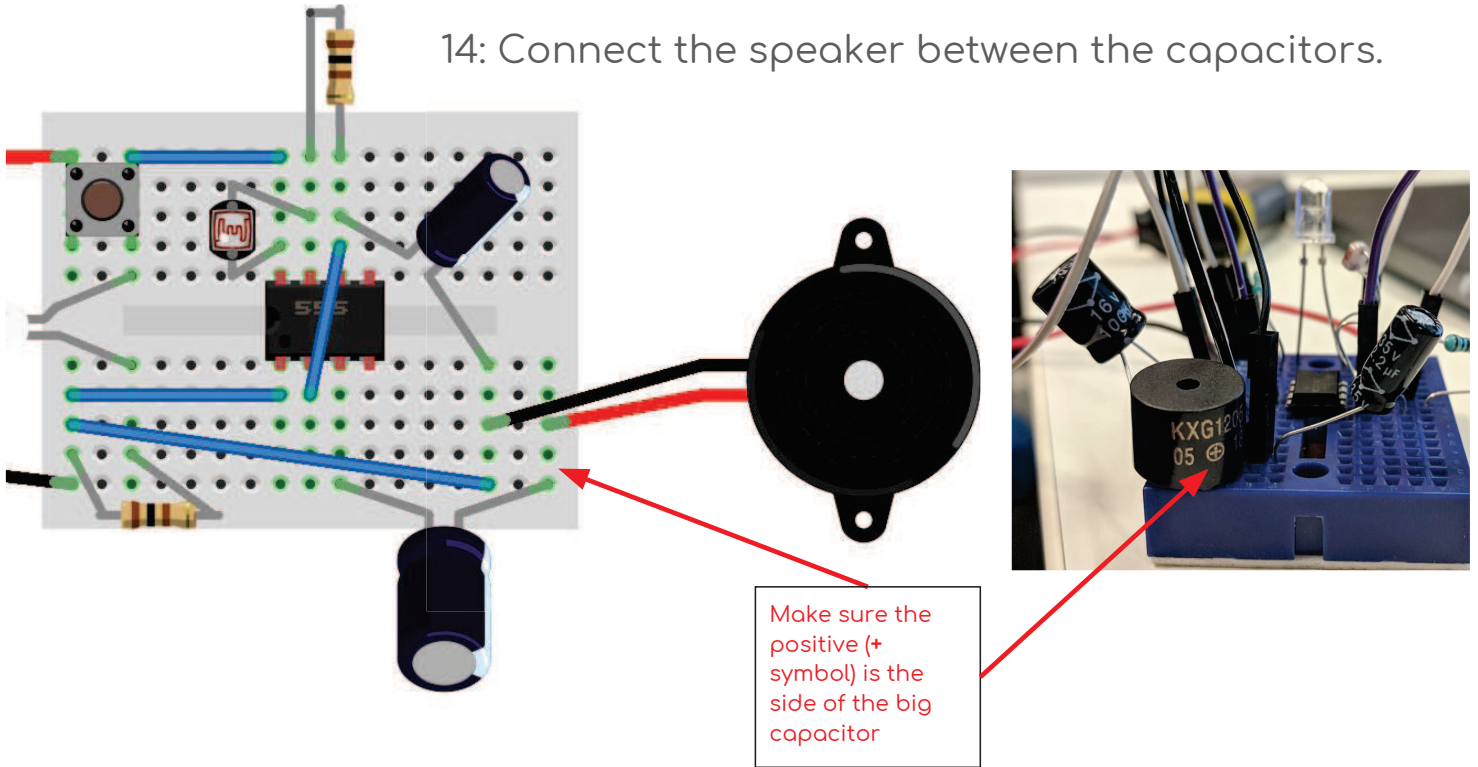
14: Connect the speaker between the capacitors.



15: Connect the battery

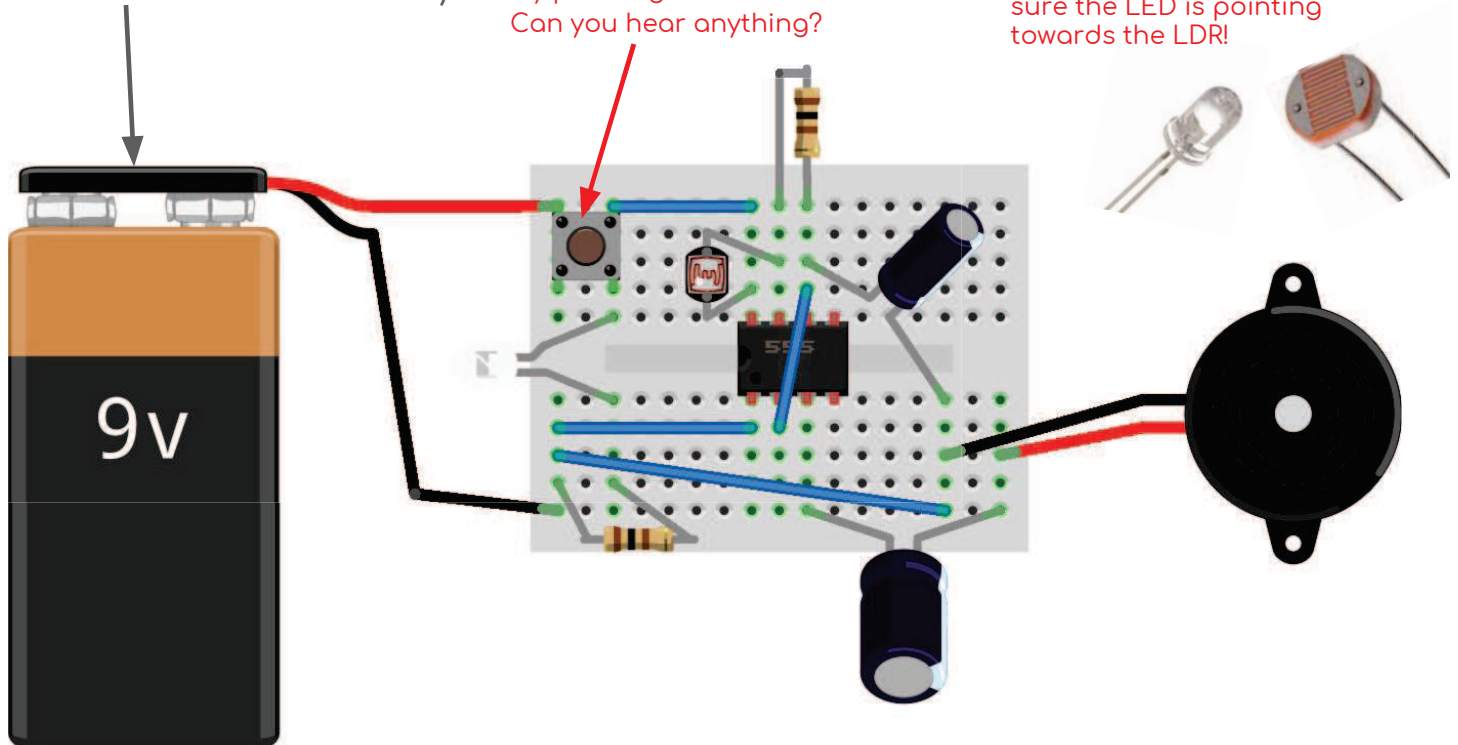

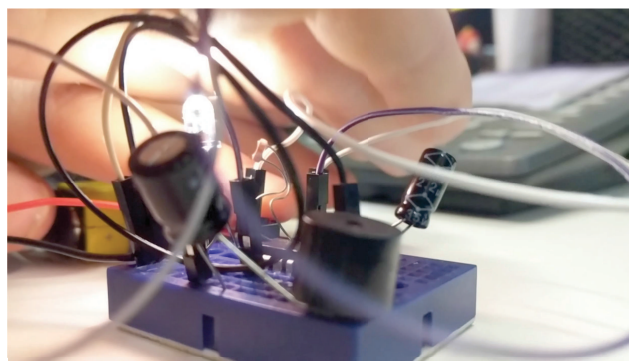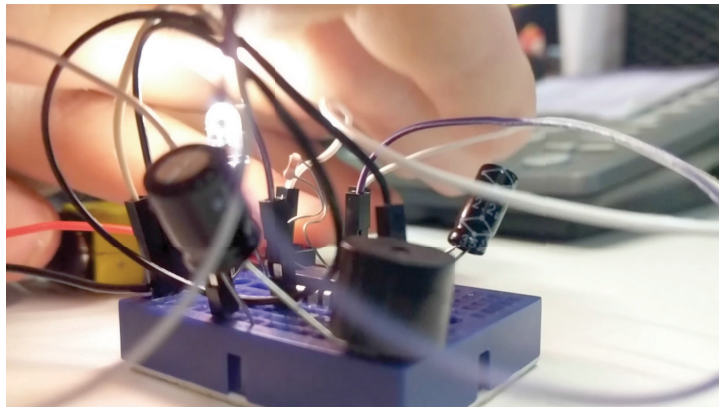16: Try waving your hand in front of the LED light while pressing the button, what do you notice?



If you've got it set up right:

- as you put your hand **closer** to the LED you're giving
- the LDR (light dependant resistor) **more light** and this causes
- its **lower resistance** and
- a **higher pitch** of your musical instrument! A higher sound.

And as you move you hand away it goes lower.